

UNIT – IV

8. (a) What is full-subtractor ? Design a full-adder and implement the same using gates. 8
- (b) What is a BCD to seven-segment Decoder ? Design and implement it. 8
9. Explain the following :
- (a) Code Converters 8
- (b) Comparators 8

Roll No.

97664

BCA 1st Semester (New)

Examination – November, 2017

LOGICAL ORGANIZATION OF COMPUTER - I

Paper : BCA-104

Time : Three Hours]

[Maximum Marks : 80

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Question No. 1 is *compulsory*. Attempt *four* questions by selecting *one* question from each Unit. All questions carry equal marks.

1. (a) What is a multiplexer ? Outline its relevance.

$2 \times 8 = 16$

- (b) What is Unicode ? State its relevance.
- (c) What are Demultiplexers ? State their importance.
- (d) What are digital signals ? Explain.
- (e) What is the smallest and largest integer number represented in a 32-bit computer ?

- (f) What are Venn Diagrams ?
- (g) Prove $x.y' + y.z' + z.x' = x'.y + y'.z + z'.x$, algebraically.
- (h) What are encoders ?

UNIT – I

- 2. (a) Which number system is followed in digital computers and why ? 4
- (b) Find out the values of X, Y and Z in the following :
 $(108.750)_{10} = (X)_2 = (Y)_8 = (Z)_{16}$ 12
- 3. Explain the following :
 - (a) Error detection and correction codes 8
 - (b) Character Codes 8

UNIT – II

- 4. (a) What are De-Morgan's Law ? Illustrate. 6
- (b) Kush wants to purchase a bicycle. The bicycle must have brakes. He will buy a bicycle that has either a hand-brake or a foot-brake. No bicycle has both types. Write the Boolean equation for buying a bicycle. Implement the same using basic gates. 10

5. Explain the following :

- (a) Duality principle 6
- (b) Canonical forms of Boolean Functions 5
- (c) Boolean Axioms 5

UNIT – III

- 6. (a) What are Universal Gates ? Why these are named so ? Justify. 6
- (b) What do you mean by multilevel NAND and NOR circuits ? Illustrate. 5
- (c) What are AND-OR-INVERT and OR-AND-INVERT implementation ? Explain. 5
- 7. (a) What is combinational circuit ? What are its characteristics ? Detail out the procedure for design of combinational circuit. 8
- (b) Design a combinational circuit that receives 2-bit binary input and produces its square at the output. 8

Roll No.

97664

**BCA 1st Semester (New)
Examination – November, 2018
LOGICAL ORGANIZATION OF COMPUTERS-I**

Paper : BCA-104

Time : Three Hours]

[Maximum Marks : 80

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *four* questions by selecting *one* question from each Unit. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (a) What is BCD adder ? $2 \times 8 = 16$
(b) What is meant by digital logic ? Explain.
(c) What is the difference between Boolean Algebra and Real Algebra ?
(d) Which number system is followed in digital computers and why ?
(e) What are Demultiplexers ? State their importance.
(f) What is Unicode ? State its relevance.
(g) What is the smallest and largest integer number represented in a 32-bit computer ?
(h) What are code converters ?

97664-7,350-(P-3)(Q-9)(18)

P. T. O.

UNIT – I

2. (a) What are parity bits ? How are these relevant in error-detection and correction codes ? Illustrate through suitable examples. 7
- (b) Find out the values of X, Y and Z in the following : 9
- $(75.75)_{10} = (X)_2 = (Y)_8 = (Z)_{16}$
3. Explain the following :
- (a) Floating-point Representation of numbers 8
- (b) Character codes 8

UNIT – II

4. (a) What is principle of Duality ? Illustrate. 6
- (b) Simplify the following Boolean expression using K-map : 10
- $F(a,b,c) = \Sigma(1,4,5,6,7)$
- and realize the same using NAND gates.
5. Explain the following :
- (a) SOPs and POSs 5
- (b) Venn diagrams 5
- (c) Boolean Algebra 6

UNIT – III

6. (a) What are Universal Gates ? Why these are named so ? Justify. 6
- (b) Design a combinational circuit that receives 4-bit binary input and produces its 2's complement. 10

7. (a) What do you mean by multilevel NAND and NOR circuits ? Illustrate. 4
- (b) What are AND-OR-INVERT and OR-AND-INVERT implementation ? Explain. 4
- (c) What is combinational circuit ? What are its characteristics ? Detail out the procedure for design of combinational circuit. 8

UNIT – IV

8. (a) What is a multiplexer ? How does it work ? What are its applications ? Explain. 8
- (b) What is a full-adder ? Design a full-adder and implement the same using gates. 8
9. Explain the following :
- (a) BCD to seven-segment Decoder 8
- (b) Magnitude Comparators 8